

23#: 31, 36, 45, 53

31 Look at 23-9 but use σ and subtract hole

~~$\frac{dq}{Q} = \frac{2\pi r dr}{(\pi R_2^2 - \pi R_1^2)}$~~

$$Q = \sigma A = \sigma (\pi R_2^2 - \pi R_1^2)$$


$$\text{so } \frac{dq}{\sigma} = 2\pi r dr$$

$$V = \frac{1}{4\pi\epsilon_0} (2\pi\sigma) \int_0^{R_2} \frac{r dr}{(x^2 + r^2)^{1/2}} \quad (\text{disk})$$

(hole)

$$- \frac{1}{4\pi\epsilon_0} (2\pi\sigma) \int_0^{R_1} \frac{r dr}{(x^2 + r^2)^{1/2}}$$

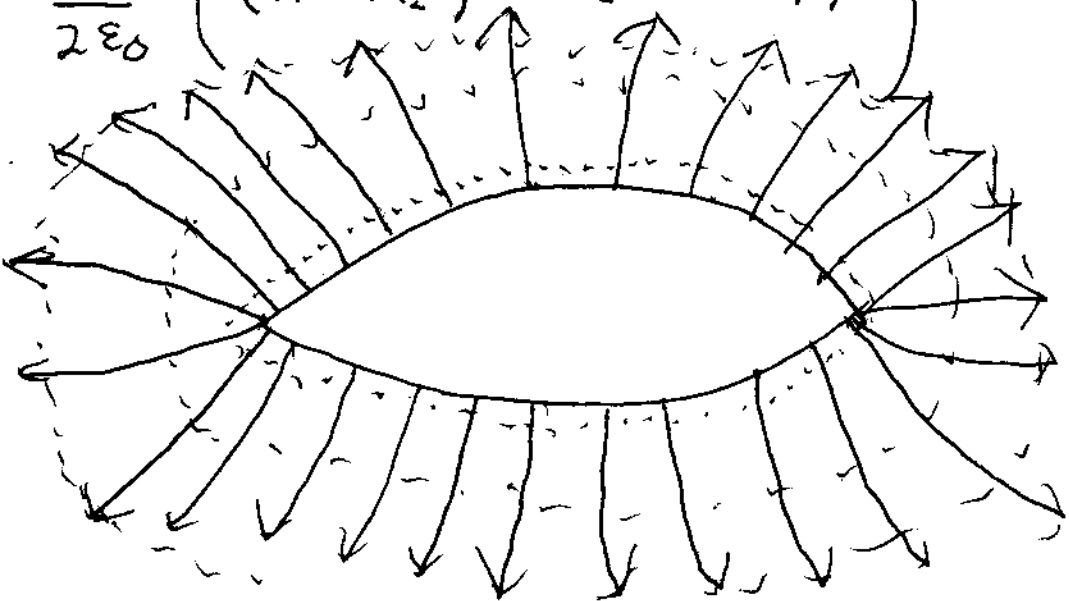
$$= \frac{\sigma}{2\epsilon_0} \left((x^2 + R_2^2)^{1/2} - (x^2 + R_1^2)^{1/2} \right)$$



36

$$45) V = \left(\frac{1}{4\pi\epsilon_0} \right) \frac{Q}{r} \quad \vec{E} = -\frac{dV}{dr} \hat{r} \quad \text{if } \hat{r} \parallel \vec{E}$$
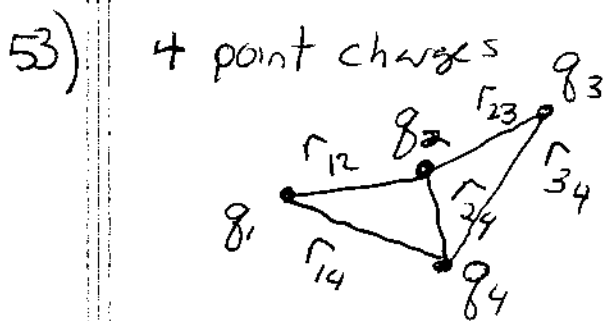
$$\text{so } E = -\frac{d}{dr} \left(\frac{1}{4\pi\epsilon_0} \frac{Q}{r} \right) = \frac{1}{4\pi\epsilon_0} \frac{Q}{r^2} \checkmark$$



$$U = \frac{Kq_1q_2}{r_{12}} + \frac{Kq_1q_3}{r_{13}}$$

$$+ \frac{Kq_1q_4}{r_{14}} + \frac{Kq_2q_3}{r_{23}} + \frac{Kq_2q_4}{r_{24}} + \frac{Kq_3q_4}{r_{34}}$$

6 terms!

(5 charges would have 10 terms)

$$24-5) Q = CV \quad \Delta Q = C \Delta V \rightarrow 16 \mu C = C (28V) \\ C = .57 \mu F$$


$$7. Q = CV = C \left(\frac{W}{q} \right) = 2.0 C$$

24-11) $V = \frac{Q}{4\pi\epsilon_0 r^2 E}$ SO $C = \frac{Q}{V} = 4\pi\epsilon_0 r^2 E = 7.1 \times 10^{-4} F$

21 in series

$$\frac{1}{1600 \text{ pF}} = \frac{1}{3600 \text{ pF}} + \frac{1}{X}$$
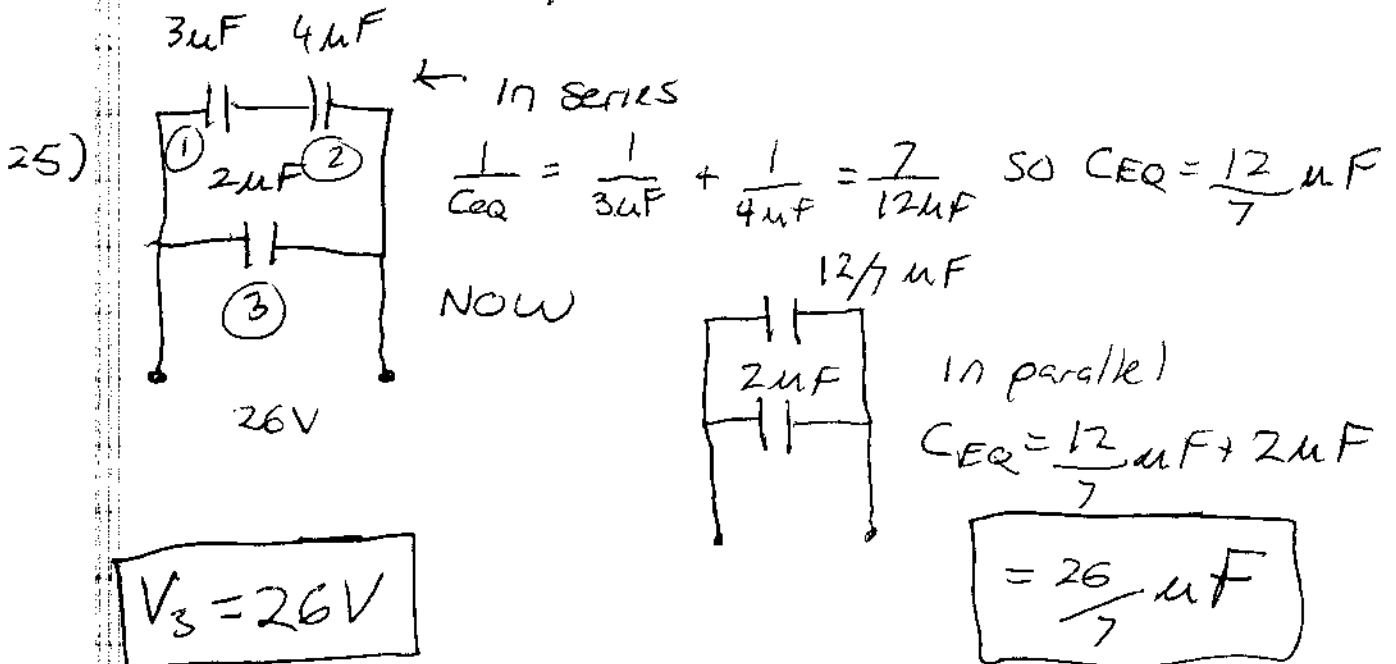
$$\frac{6.25 \times 10^{-4}}{\text{pF}} = \frac{2.78 \times 10^{-4}}{\text{pF}} + \frac{1}{X} \quad X = 2880 \text{ pF}$$



$$Q = CV = (2\mu F)(26V) = 52 \mu C$$


$$V_1 + V_2 = 26V \quad Q_1 = Q_2 \text{ so } C_1 V_1 = C_2 V_2$$

$$V_1 + \frac{C_1}{C_2} V_1 = 26V$$


$$\frac{7}{4} V_1 = 26V \quad V_1 = 14.86V \quad V_2 = 11.14V$$

$$Q_1 = Q_2 = C_1 V_1 = 44.6 \mu C$$

33)

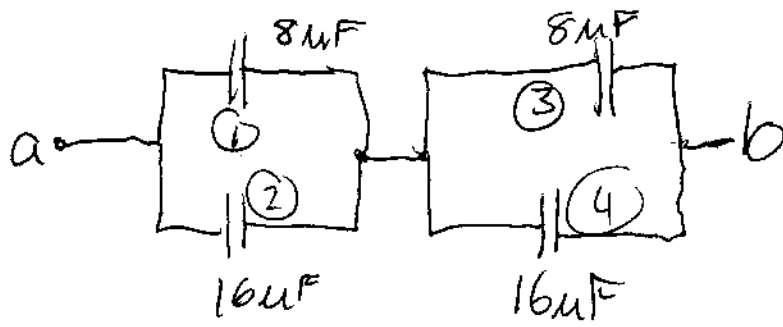


$16 + 8 = 24$

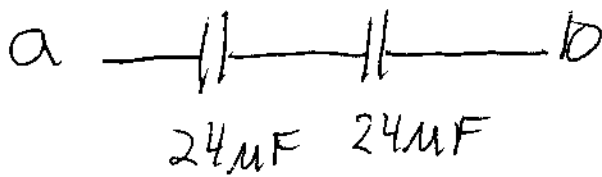

$\frac{1}{24} + \frac{1}{24} = \frac{2}{24}$

$C_{EQ} = 12\mu F$

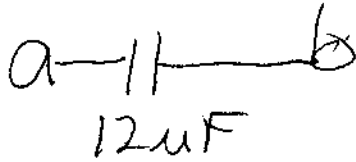

$Q_3 = 30\mu C = Q_1$

$Q_{12} = Q_{34}$

$V_{12} = V_{34} \quad V_{AB} = V_{12} + V_{34}$

$V_{AB} = \frac{Q_{AB}}{C}$

$V_3 = V_4 \quad \frac{Q_3}{C_3} = \frac{Q_4}{C_4} \quad \frac{30\mu C}{8\mu F} = \frac{Q_4}{16\mu F}$

$Q_4 = 60\mu C$
 $Q_2 = 60\mu C$

$V_3 = V_1 = \frac{30\mu C}{8\mu F} = 3.75V \quad \checkmark$

$V_2 = V_4 = \frac{60\mu C}{16\mu F} = 3.75V$

$V_{AB} = 7.5V$

24-45) In parallel:

$$C_1 + C_2 = .35 \mu\text{F}$$

$$U = \frac{1}{2} CV^2 = 2.5 \times 10^{-5} \text{ J}$$

In series:

$$\frac{1}{C_{\text{EQ}}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{.15 \mu\text{F}} + \frac{1}{.20 \mu\text{F}} = \frac{6.67}{\mu\text{F}} + \frac{5}{\mu\text{F}}$$

$$\text{so } C_{\text{EQ}} = .0857 \mu\text{F}$$

$$U = \frac{1}{2} CV^2 = 6.2 \times 10^{-6} \text{ J}$$

Charge $Q = CV$

$$\text{parallel} = (.35 \mu\text{F})(12\text{V}) = 4.2 \mu\text{C}$$

$$\text{series} = (.0857 \mu\text{F})(12\text{V}) = 1.0 \mu\text{C}$$

55) $U = \frac{1}{2} Q^2 / C$

$$U/U_0 = \frac{C_0}{C} = \frac{1}{K} \quad \text{so } U = U_0 / K = \frac{2.33 \times 10^3 \text{ J}}{7} = 330 \text{ J}$$

ch 25

5) $V = IR = 750V$

9) $V = IR$ so $R = \frac{V}{I} = 16\Omega$

$I = \frac{\Delta Q}{\Delta t}$ so $\Delta Q = I \Delta t = 7.5A (15m) \left(\frac{60s}{min}\right)$
 $= 6.8 \times 10^3 C$


26

#7

$R_{series} = 25\Omega + 70\Omega = 95\Omega$


$\frac{1}{R_{parallel}} = \frac{1}{25\Omega} + \frac{1}{70\Omega} = \frac{.0543}{\Omega}$

so $R_{parallel} = 18.4\Omega$

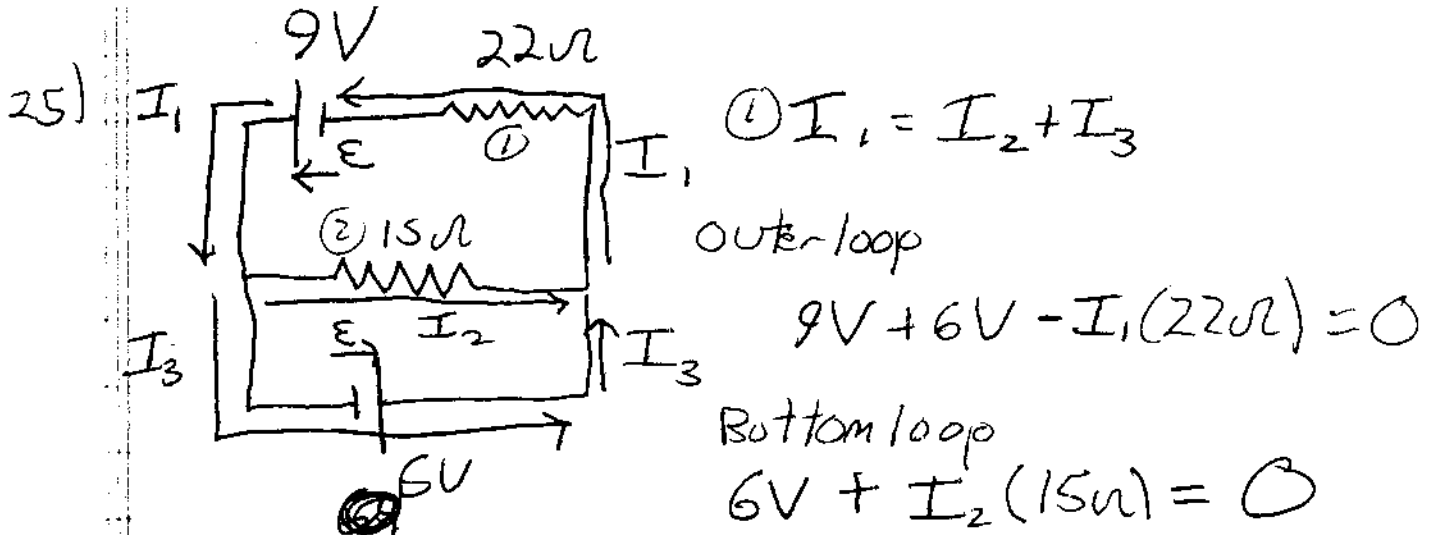

$I_1 = .68A$ $I_2 = -.4A$

so $I_3 = +1.08A$

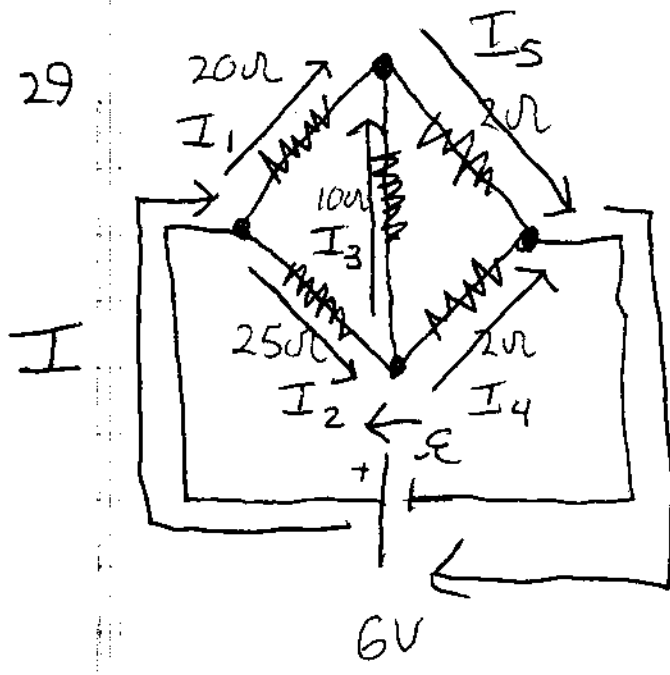

$$I = I_1 + I_2$$

$$I_2 = I_3 + I_4$$

$$I = I_5 + I_6$$

$$I_4(2\Omega) + I_2(25\Omega) - I_1(20\Omega) - I_5(2\Omega) = 0$$

Top

$$-I_1(20\Omega) - I_5(2\Omega) + 6V = 0$$

Bottom

$$-I_2(25\Omega) - I_4(2\Omega) + 6V = 0$$

Left

Triangle

$$-I_1(20\Omega) + I_3(10\Omega) + I_2(25\Omega) = 0$$

Right triangle

$$-I_5(2\Omega) + I_4(2\Omega) - I_3(10\Omega) = 0$$